

CMPSC 210
Principles of Computer Organization
Fall 2016

John Wenskovitch

<http://cs.allegheny.edu/~jwenskovitch/teaching/CMPSC210>

Lab 9 – Logisim
Due (via Bitbucket) Wednesday, 30 November 2016
30 points

Lab Goals

- Practice creating circuits using Logisim, and designing those circuits using truth tables.
- Practice using truth tables and Karnaugh maps in general to solve Boolean expression problems in both directions.

Assignment Details

This assignment is broken in two major components. The first component is a tutorial for building more complex circuits using Logisim. The second component is back to the mathematical response style from earlier in the semester, requesting that you solve problems using Boolean logic.

Part 1: Grandma Ann’s Cookie Watcher (20 points)

Grandma Ann, owner and founder of Grandma Ann’s Crumbling Cookies, recognizes that to stay competitive in today’s marketplace, she must integrate technology into her business in order to keep quality up and prices down.

To assist her business, she enrolled in CMPSC 210 last year. Using her acquired knowledge, she designed a cookie watcher. The cookie watcher “watches” multiple batches of cookies baking simultaneously. It is precisely timed to an individual recipe’s cooking time. The cookie watcher alerts an employee to when a batch is ready to be taken out of the oven, as well as when a batch is ruined (overcooked). It is easily scalable to watch multiple cookie batches at once. Thanks to the cookie watcher, fewer cookies are being burnt, and the cookies are consistently baked the proper amount of time. As a result, Grandma Ann’s profits soared. She has since retired to a private island in the Antilles.

In this section of the lab, you will recreate her cookie watcher circuit in Logisim. Naturally, Grandma Ann first tested her design in Logisim and then eventually soldered her own physical version. First, look at the final design on the next page.

 


Figure 1: The CookieWatcher subcircuit. One input is whether that batch of cookies was handled. The other input is the clock signal. The inputs are fed into a counter. The counter's value is used to determine whether the cookies are done and whether they are ruined (overbaked).

Now start the following steps:

1. Start a new Logisim circuit up.
2. Click "Project" then "Add Circuit" to add a subcircuit. We can design a subcircuit once, then instantiate multiple copies of it. Name this subcircuit "CookieWatcher." We will first design this circuit. It will be capable of watching exactly 1 batch of cookies.
3. Add 2 input pins and give them the proper labels.
4. Add a counter (available from the "Memory" section on the side). Change its "Action on Overflow" property to be "Stay on Value." When the counter reaches its maximum, it will not wrap around back to 0. Change its "Data Bits" to 10.
5. Connect the input pins to the counter as shown in the CookieWatcher design.
6. Draw a short wire coming out of the "Q" output of the counter. This is the counter's value. The output is, by default, a bundle. A bundle is several (in this case 10) wires all connected together. Using a bundle can save us space when working with multiple bits at once. Bundles are always black in color, and we are unable to see the values on the individual wires within the bundle.
7. Connect a splitter (from the "Wiring" category) to the end of the bundle. Change the splitter's BitWidthIn to 10 (because the counter's output is 10 bits). Change the splitter's FanOut to be 10. This will split the 10-bit input into 10 pieces. A 10-bit input split 10 ways will result in 10 1-bit outputs.
8. Connect the 10 outputs from the splitter to AND gates as shown. Connect the AND gates as shown.

9. Add 2 output pins and give them the names as shown. The CookieWatcher's output is whether the batch of cookies it is watching is done (1 of the output pins states this) as well as whether that batch has been burnt (the other output pin states this).
10. Before moving on, think about the circuit you've just built. Why are the outputs from the counter connected up in the way that they are? What do you think will happen as the counter changes? When will the outputs of the cookie watcher become true? False?

You have now completed the CookieWatcher circuit. Now, we can connect multiple CookieWatchers to create an automated cookie baking notification system capable of watching any number of baking cookies. Switch to the “main” circuit, which should currently be blank. To do this, double-click on the word “main” (which should be above the words “CookieWatcher” on the left hand pane).

1. Add a clock component (available in the “Wiring” category).
2. Add 6 buttons (available from the “Input/Output” category).
3. Add 6 CookieWatcher subcircuits. To insert one subcircuit, single-click on the “CookieWatcher” entry in the side pane. Then, click in the main circuit to place it somewhere. It will appear as a small box. Do this 6 times.
4. With the arrow tool active, however over the four dots on a CookieWatcher circuit. Notice that the left-hand ones are blue, meaning that they are unconnected, expecting an input. The right-hand ones are dull green right now, meaning that they are outputting a 0. We call these dots pins. Hovering over a pin tells you the purpose of the pin, assuming you have the subcircuit's pin a label. For example, hovering over the top pin on the right-hand side of a CookieWatcher should show that the pin is the CookiesRuined pin.
5. Add 8 LEDs (under “Input/Output”). Connect them as shown in the figure.

Your circuit should now be done. To test it, we will force the clock to tick, thus updating the circuit state. We can **poke** the clock to have it switch from low (0) to high (1) and vice versa. This lets us step through time, one cycle at a time.

To really test this circuit though, let's force the clock to update automatically at some fixed frequency. Under the “Simulate” menu, go to “Ticks Frequency” and select “128 Hz” (128 Hertz, 128 times per second).

Now, under “Simulate” choose “Ticks Enabled” (keyboard shortcut Ctrl-K). The clock will automatically tick away, advancing the circuit state.

The clock is connected to each CookieWatcher, and the CookieWatcher circuit will, eventually, turn on the lights. At 128Hz, the bottom light should come on in about 4 seconds. The bottom light turning on informs the employee that a batch of cookies are done. The employee would then take out the cookies, put in a new batch, and press (i.e. poke) the batch's button to reset the timer.

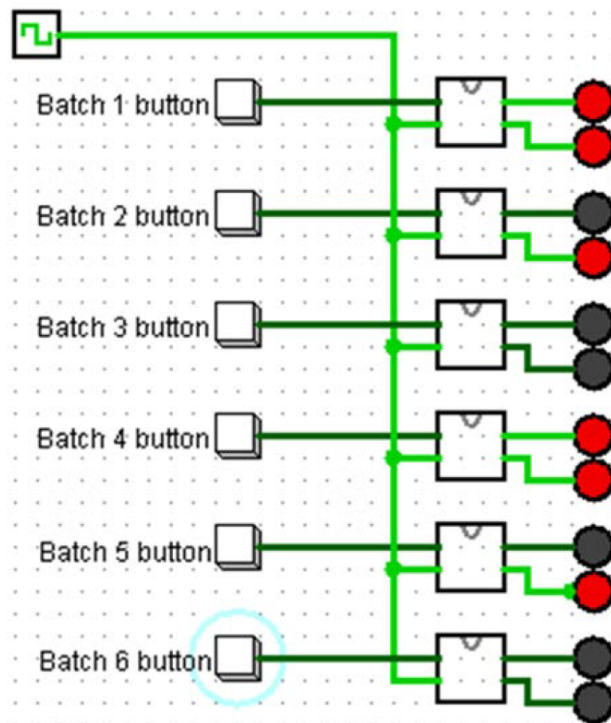


Figure 2: Six cookie watchers. The second and fifth batches are ready to be taken out of the oven. The first and fourth batches are burnt. The third and sixth batches are not ready to be taken from the oven.

If the employee waits too long, the top light will come on. This lets the employee know that the cookies have been burnt. The employee should then put in a new batch, throw out the old batch, and press the reset button. At a blockrate of 128Hz, the top light will come on after 8 seconds.

Make sure that your circuit is working as designed. You should understand what each of the components are doing and why they are doing what they do.

Ask yourself the following (you do not have to submit these answers):

- When exactly does the CookiesDone light turn on?
- When exactly does the CookiesRuined light turn on?
- When the user pokes a button, what happens? How does the counter respond?

Part 2: Solving Boolean Expressions (10 points)

1. Construct a truth table for the expression $Z = \sim [(A|B) \& (\sim A|C)] | (B \& \sim C)$ (and ignore the absurd spacing that LaTeX decided to put into this expression...).
2. Take the output of the truth table from the previous question, and simplify the expression using a Karnaugh Map. (Depending on the structure of your K-Map and your simplifica-

tion process, you may arrive at an identical expression or something different but logically equivalent.)

Submission Details

For this assignment, your submission to your BitBucket repository should include the following:

1. Your Cookie Watcher Logisim file.
2. Your responses to the questions in Part 2. [If you have hand-written the solutions to these exercises, please submit them to TA Victor Zheng instead of BitBucket.]

Before you turn in this assignment, you also must ensure that the course instructor has read access to your BitBucket repository that is named according to the convention `cs210f2016-<your user name>`.